



(All Rights Reserved)

UNIVERSITY OF GHANA
SECOND SEMESTER EXAMINATIONS, 2013/2014
LEVEL 300: BACHELOR OF SCIENCE IN ENGINEERING
CPEN 306: MICROELECTRONICS DEVICES AND CIRCUITS

INSTRUCTIONS: Answer ALL five (5) questions.

Time Allowed: THREE (3) hours

Q1. (a) Draw a single stage common emitter amplifier using a voltage divider biasing network. [4 marks]

(b) Given that the voltage divider network is formed by resistors R_1 and R_2 , and that the values of $R_1 = 20k\Omega$ and $R_2 = 40k\Omega$. If the power supply $V_{cc} = 10V$ and the load resistor is $12k\Omega$ whilst the resistor connected to the emitter is $10k\Omega$, calculate the:

- (i) quiescent base voltage.
- (ii) quiescent base current.
- (iii) required capacitance of the capacitor needed at the emitter terminal to ensure d.c stabilization if the signal frequency ranges from 100Hz to 20kHz. [12 marks]

(c) Explain why the potential divider bias network is mostly preferred to other biasing arrangement. [2 marks]

(d) Explain the term -3dB bandwidth as applied to amplifiers. [2 marks]

Q2. Define the following parameters of power supply systems:

- (a) (i) Efficiency of rectification. [2 marks]
- (ii) Ripple factor. [2 marks]
- (iii) Peak inverse voltage (PIV). [2 marks]

(b) A single-phase full-wave rectifier uses a power transformer whose secondary voltage is 220V r.m.s. The load resistor is $25k\Omega$. Neglect the transformer losses and the forward drops in the diodes. Determine the following:

- (i) d.c output voltage. [4 marks]
- (ii) ripple voltage. [4 marks]
- (iii) PIV. [4 marks]

- (c) What is the distinct advantage of bridge rectifier circuit over the normal full-wave rectifier circuit? [2 marks]

Q3. (a) Draw the small signal **h-parameter** equivalent of a common-emitter amplifier circuit. [3marks]

- (b) A common-emitter amplifier has the following **h-parameters**:

$$h_{fe} = 100; h_{oe} = 200\mu S; h_{re} = 160 \times 10^{-6}; R_L = 24k\Omega,$$

Calculate the following:

- (i) Current gain, A_i . [2marks]
- (ii) Input resistance, r_{ie} . [2marks]
- (iii) Voltage gain, A_v . [2marks]

- (c) With the aid of a circuit diagram, explain how a transistor can be used as an electronic switch. [5 marks]

- (d) A switching NPN silicon transistor has a forward current gain, $\beta = 100$ and maximum collector current, $I_{MAX} = 10mA$. If the input voltage is $12V$, calculate the base resistor needed to switch the load "fully ON". [6 marks]

Q4. (a) A $6V$ d.c stabilized power supply needed to operate a computer is to be produced from a $15V$ full-wave bridge rectifier using a Zener diode as the regulator circuit. The maximum power rating of the Zener diode, P_Z is $4W$. Calculate the following:

- (i) maximum current flowing through the Zener diode. [3marks]
- (ii) value of the series current limiting resistor, R_S . [3 marks]
- (iii) load current, I_C if a load resistor of $2k\Omega$ is connected across the Zener diode. [3 marks]
- (iv) total supply current, I_S . [3 marks]

- (b) Give three (3) advantages of CMOS ICs over other types of ICs. [3 marks]

- (c) What is the main difference between Depletion-type MOSFETs and the Enhancement-type MOSFETs? [3 marks]

- (d) Explain the Zener breakdown phenomenon associated with semiconductor diodes when the reverse bias voltage applied across them are increased beyond the breakdown point. [2marks]

Q5. (a) Draw a circuit diagram of a single-stage n-channel FET amplifier and explain the effects of negative gate voltage and positive drain voltage on drain current. [6marks]

- (b) Define the FET parameter transconductance (g_m). [2marks]

- (c) Draw a frequency response curve of a resistance-capacitance coupled amplifier and explain the causes of the sudden drop in amplification at the low and high frequency ranges. [6marks]

- (d) Determine the voltage and power gain in decibel (dB) of an amplifier with an input signal of $1mA$ at $10mV$ and corresponding output signal of $10mA$ at $1V$. [6marks]