




(All Rights Reserved)

**UNIVERSITY OF GHANA**  
**SECOND SEMESTER EXAMINATIONS, 2013/2014**  
**LEVEL 200: BACHELOR OF SCIENCE IN ENGINEERING**  
**CPEN 206: LINEAR CIRCUITS**

**INSTRUCTIONS:** Answer ALL five (5) questions.


Time Allowed: THREE (3) hours

- Q1.** (a) State the **Maximum Power Transfer** theorem. [2marks]  
(b) If a voltage source of e.m.f,  $E_S$  with internal impedance of  $R_S + jX_S$  is connected to a load of impedance  $R_L + jX_L$ , prove that the maximum possible transfer of power from the source to the load will occur when the source and the load impedances are of the same magnitude. [8marks]  
(c) For the circuit shown in *figure 1* below, calculate the value of the load resistor,  $R_L$  for which the power dissipated in it would be **maximum** and find the power. [10marks]

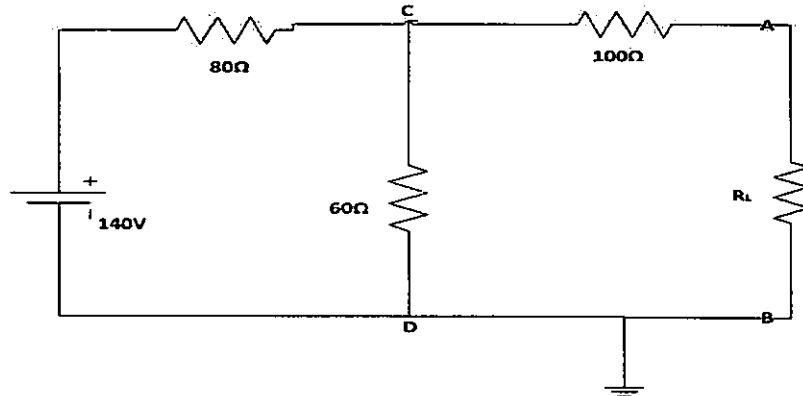

*Figure 1.*

- Q2.** (a) State **Norton's** theorem. [2marks]  
(b) Using **Norton's** theorem, calculate current flowing in a **200Ω** resistor connected across terminals **AB** of the circuit shown in *figure 2* below. [10marks]

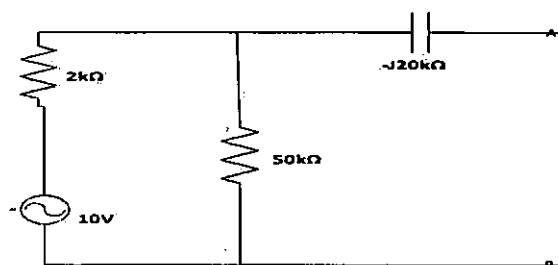

**Figure 2.**

(c) Verify your answer by using **Thevenin's** theorem. **[8marks]**

**Q3. (a)** Draw a block diagram of an Operational amplifier. **[3marks]**

(b) Give **four (4)** special characteristics (parameters) that an Operational amplifier should have. **[4marks]**

(c) Define an **operational amplifier bandwidth** and draw the Voltage gain (dB) / Frequency (Hz) response curve. **[4marks]**

(d) A non – inverting operational amplifier has input resistance  $R_i = 40\text{k}\Omega$ , feedback resistance,  $R_f = 200\text{k}\Omega$  and load resistance,  $R_L = 10\text{k}\Omega$ . If a voltage of 6V is applied to the input, calculate:

(i) The output voltage ( $V_o$ ). **[3marks]**

(ii) The voltage gain ( $A_v$ ). **[3marks]**

(e) Draw an integrator circuit using an operational amplifier. **[3marks]**

**Q4. (a)** Give **two (2)** advantages of Active Filters over Passive Filters. **[2marks]**

(b) Using the **Voltage Potential Divider** theory, show how a Passive Low Pass Filter (LPF) can easily be made by connecting together in series a single resistor with a single capacitor. **[6marks]**

(c) A low pass filter circuit consists of a resistor of  $100\text{k}\Omega$  in series with a capacitor of  $70\text{nF}$  and input voltage ( $V_{in}$ ) of 10V. Calculate the output voltage ( $V_o$ ) at frequency of 400Hz and again at frequency of 50kHz. **[6marks]**

(d) Use the result obtained in Q4 (c) to plot the output voltage against different values of the input frequency, frequency response curve and explain by the curve how the network acts as a Low Pass Filter. **[6marks]**

**Q5. (a)** A current of 500mA flows in an inductor of 60mH, and  $10\Omega$  resistance. Calculate the voltage across the inductor at a frequency of 1000Hz. **[6marks]**

(b) A 10uF capacitor is charged from a 24 V d.c supply and is then disconnected from the supply. Calculate the energy stored in the capacitor. **[7marks]**

(c) A capacitor which is formed by nine (9) metal plates and have air as its dielectric. The area of the plate is  $0.05\text{cm}^2$  and the distance between the plates is 0.06cm. Calculate the value of the capacitor given permittivity of free space ( $\epsilon_0$ ) =  $8.85 \times 10^{-12}$  F/m. **[7marks]**