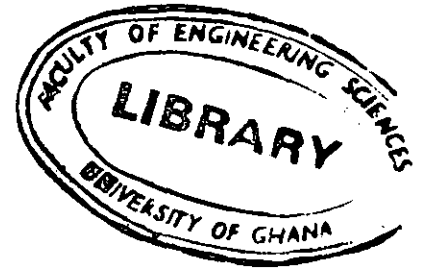




UNIVERSITY OF GHANA

(All Rights Reserved)



**BACHELOR OF SCIENCE IN ENGINEERING
SECOND SEMESTER EXAMINATION, 2015/2016
DEPARTMENT OF COMPUTER ENGINEERING
CPEN 302: COMPUTER SYSTEMS ENGINEERING (3 CREDITS)**

INSTRUCTIONS:

ANSWER ALL QUESTIONS. ALL ABBREVIATIONS HAVE THEIR USUAL MEANING.

TIME ALLOWED: TWO AND HALF (2 1/2) HOURS

1.

Consider Fig. 1 below; Node B is pre-charged by device M1. The signal on line A falls 2.5V with transition time $t_r = 300$ ps pulling signal B downward through the coupling capacitance C_c . The $0.5 \mu\text{m}/0.35 \mu\text{m}$ keeper is in the resistive region with a resistance of about $4.6 \text{ k}\Omega$. The parasitic capacitance of node B, C_o , is about 20pF , and the coupling capacitance, C_c is 10 pF .

- a. Determine the system time constant. (2 Marks)
- b. Evaluate ΔV_B assuming there is no keeper. (2 Marks)
- c. Evaluate ΔV_B in the presence of keeper M2 for $t=3\tau_{xp}$ (4 Marks)

Note:

$$V_B(t) = \begin{cases} k_c \left(\frac{\tau_{xp}}{t_r} \right) \left[1 - \exp \left(-\frac{t}{\tau_{xp}} \right) \right] & \text{if } t < t_r \\ k_c \left(\frac{\tau_{xp}}{t_r} \right) \left[\exp \left(-\frac{t-t_r}{\tau_{xp}} \right) - \exp \left(-\frac{t}{\tau_{xp}} \right) \right] & \text{if } t \geq t_r \end{cases}$$

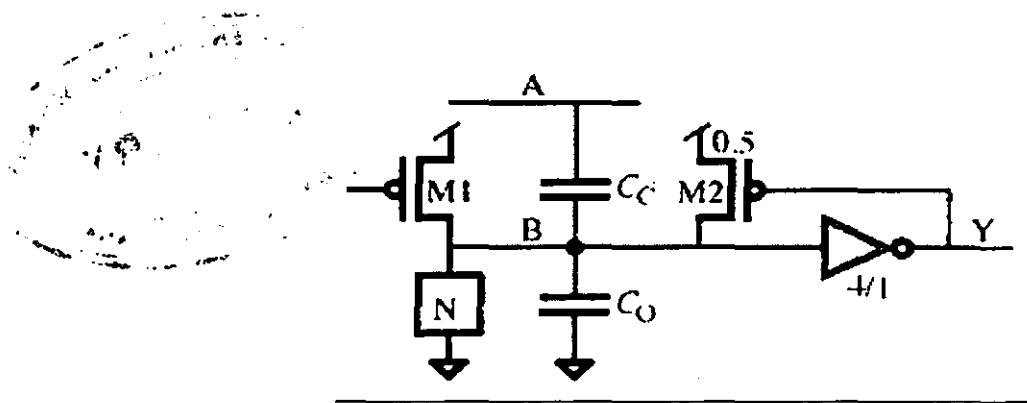


Fig. 1. Cross-talk of a precharged circuit with a keeper

- d. Explain the following categories of cross-talk with the aid of diagrams and provide three countermeasures for each of them

i. Near and Far-end cross talk **(5 Marks)**

ii. Signal return cross-talk **(5 Marks)**

2.

For a transmission line geometry similar to the one provided in Fig. 2, consider the following parameters: propagation velocity $v = 1.78 \times 10^8 \text{ m/s}$ and the time delay down the line connecting U1 and U2 is given as $TD = 713 \text{ ps}$.

- Calculate the steady state voltage V_{initial} , considering a source voltage of 2V, a source impedance of 75Ω and a line impedance of 50Ω . **(2 Marks)**
- Calculate the source and load reflection coefficient considering the line is terminated in open circuit **(4 Marks)**
- Sketch the lattice diagram and the response of the lattice diagram (V_{load} and V_{source} vs time) of this undriven transmission line limited to the 5th reflection **(10 Marks)**

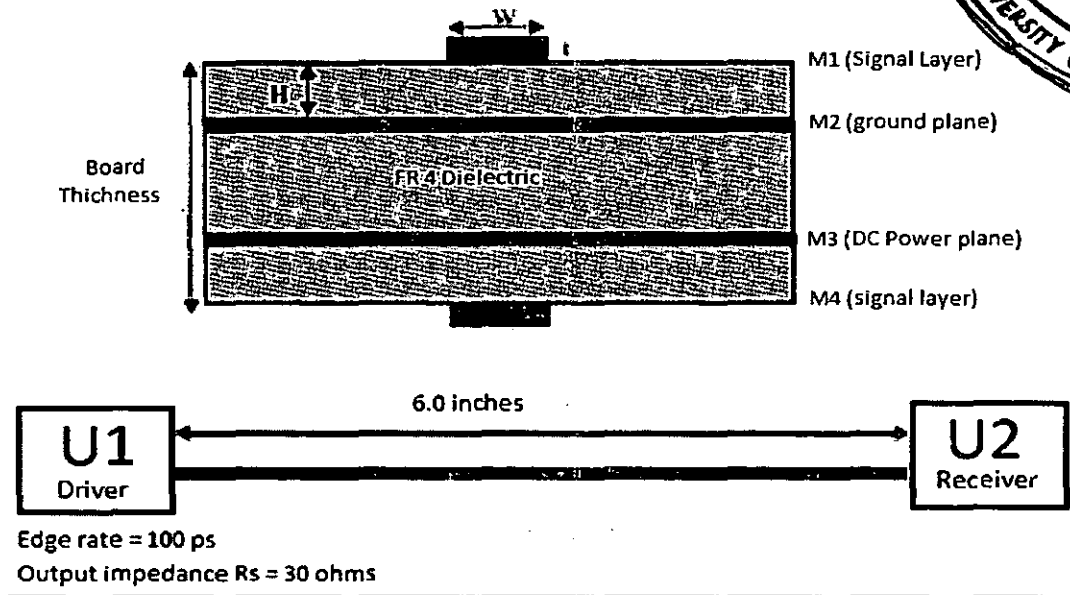


Fig. 2. Sectional view of a standard four layer motherboard stackup

3.

- With the aid of a circuit, show how overshoots are reduced in off-chip distribution networks (3 Marks)
- Explain the role of bypass capacitor for on-chip network design (2 Marks)
- Differentiate between single supply noise and differential supply noise (4 Marks)
- Based on table 1 below, if the signal swing of an SEMC is increased from 250mV to 750mV, determine the new net noise margin (6 Marks)
- Calculate the ratio of gross noise margin to noise before and after this change and comment on the results. (4 Marks)

Table 1. Noise Budget of a Digital System

Noise source	Type	Amount (%)	Amplitude (V)
Gross margin			100
Received Offset	Fixed		± 5
Receiver sensitivity	Fixed		± 5
Unrejected power supply noise	Fixed		± 5
Transmitter offset	Proportional	5	± 10
Cross talk	Proportional	10	± 20
Intersymbol interference	Proportional	15	± 30
Total noise			± 75
Net margin			25

4.

a. Differentiate between *microstrip* and *striplines*. (4 Marks)

b. With the help of the Fig. 3, show that the impedance of an infinite line is given by the equation (3 Marks)

$$Z_0 = \left(\frac{R + Ls}{G + Cs} \right)^{1/2}$$

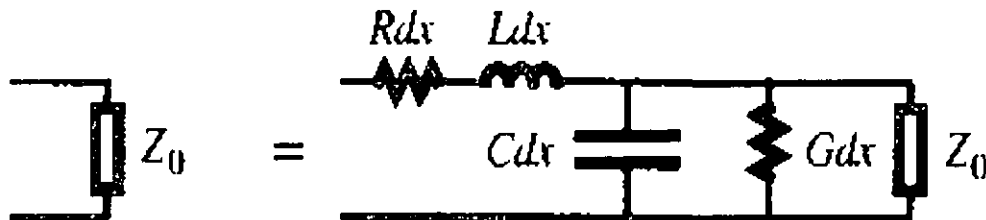


Fig. 3. Model a differential section of a transmission line

- c. Considering the standard four layer motherboard stackup model depicted in Fig.2, determine the height H for a line impedance **(2 Marks)**

$$Z_o = 50\Omega$$

Knowing

$$Z_{o_microstrip} = \frac{87}{\sqrt{\epsilon_r + 1.41}} \ln \left(\frac{5.48H}{0.8W + t} \right)$$

Assume

$$\epsilon_r = 4, t = 1$$

- d. With the help of the formula below, evaluate the effective dielectric constant, the propagation velocity and the time delay **(8 Marks)**

$$\epsilon_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left(1 + \frac{12H}{W} \right)^2 + F - 0.217(\epsilon_r - 1) \frac{T}{\sqrt{WH}}$$

$$F = \begin{cases} 0.02(\epsilon_r - 1) \left(1 - \frac{W}{H} \right)^2 & \text{for } \frac{W}{H} < 1 \\ 0 & \text{for } \frac{W}{H} > 1 \end{cases}$$

