



UNIVERSITY OF GHANA

(All rights reserved)

BACHELOR OF SCIENCE IN ENGINEERING

SECOND SEMESTER EXAMINATIONS: 2014/2015

CPEN 302 : Computer System Engineering (2 Credits)

Instructions: Attempt all questions

Time Allowed: 2 Hours

All abbreviations have their usual meaning.

QUESTION 1 (33 Marks)

- Describe the following terms:
 - Stripline (3 Marks)
 - Microstrip (3 Marks)
- Explain the phenomenon of reflection and characterize it for the following cases:
 - Line terminated in short-circuit (3 Marks)
 - Line terminated in open circuit (3 Marks)
- Describe two different tools used to solve the problem of multiple reflection with transmission line. (6 Marks)
- Develop an equivalent circuit model of loss-free transmission line 10 in. long for the cross section shown in figure 1. Assume that the driver has a minimum rise time of 2.5 ns and the dielectric constant is 4.9. Consider $H=30$ mils, $W=7$ mils, $T=0.8$ mils.

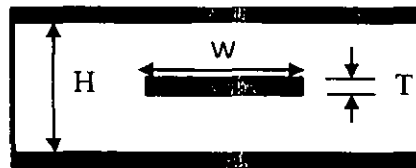


Figure 1: Model of line impedance

Note:

$$Z_o = \frac{60}{\sqrt{\epsilon_r}} \ln \left(\frac{4H}{0.67\pi(T+0.8W)} \right) \quad (15 \text{ Marks})$$

QUESTION 2 (31 Marks)

- a) Describe with the aid of diagrams, cross-talk due to:
- capacitive coupling to a floating line (3 Marks)
 - capacitive coupling to a driven capacitive line. (3 Marks)
- b) Discuss five countermeasures used to overcome transmission line cross-talk (10 Marks)
- c) Classify the following noise as either internal or external and provide a definition for each of them:
- Transmitter and receiver offset (3 Marks)
 - Power supply noise (3 Marks)
 - Timing noise (3 Marks)
 - Johnson noise (3 Marks)
 - Electromagnetic interference (3 Marks)

QUESTION 3 (36 Marks)

The attenuation of a signal travelling down a line can be modeled by the equation below:

$$V(s, x) = V(s, 0) \cdot \exp(-Ax)$$

Where A is the propagation constant given by the equation below

$$A = [(G + Cs) \cdot (R + Ls)]^{\frac{1}{2}}$$

- a) Consider the network of figure 2 which consists of the model of the transmission line and evaluate the magnitude and phase of the propagation constant A above at a frequency of 100 KHz.

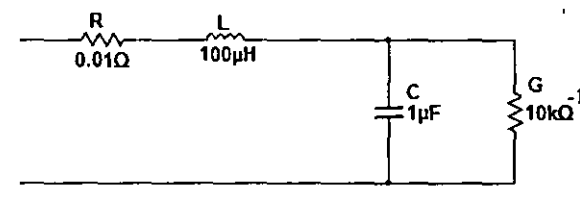


Figure 2: Model of Transmission line

(10 Marks)

- b) What happens to the signal $V(s, x)$ in the following cases
- a. Only the resistor doubles (3 Marks)

- b. Only the capacitor doubles (3 Marks)
- c. Only the inductance triples (3 Marks)
- c) Explain your observations from Q3 b) (6 Marks)
- d) Describe the following concepts:
 - Timing convention (2.5 Marks)
 - Signaling convention. (2.5 Marks)
- e) Differentiate between single supply noise and differential supply noise (6 Marks)