



UNIVERSITY OF GHANA

(All rights reserved)

BACHELOR OF SCIENCE IN ENGINEERING
SECOND SEMESTER EXAMINATIONS: 2014/2015

CPEN 306: MICROELECTRONICS DEVICES AND CIRCUITS [3 Credits]

INSTRUCTIONS: Answer ALL questions.

TIME ALLOWED: TWO AND HALF HOURS

Q1 (a) Consider the common-emitter (CE) NPN transistor amplifier shown in the figure 1 and state the function of each component in the circuit. [4marks]

(b) Given that the values of $R_1=1k\Omega$, $R_2=45k\Omega$, $R_L=40k\Omega$, $R_E=50k\Omega$ and $V_{CC}=10V$,

Calculate the:

- (i) the base voltage [2marks]
- (ii) the base current [2marks]
- (iii) the emitter current [2marks]

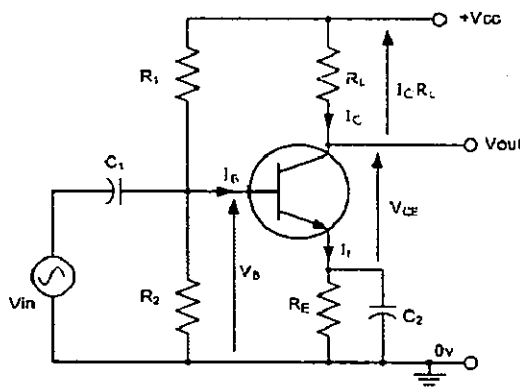


Figure 1

(c) If the input signal frequency ranges from 200Hz to 50kHz, calculate the required capacitance of the capacitor needed at the emitter terminal to ensure d.c stabilization. [4marks]

(d) Draw a frequency response curve of a resistance-capacitance coupled amplifier and explain the causes of the sudden drop in amplification at the low and high frequency ranges. [4marks]

(e) Define the term -3dB Bandwidth of an amplifier.

[2marks]

Q2.(a) Draw the static I-V characteristics of a diode and use it to explain the Zener breakdown phenomenon associated with semiconductor diodes. [4marks]

(b) A 12V stabilized voltage needed to run a d.c motor is to be produced from a full-wave bridge rectifier with an unregulated output of 25V d.c. If a Zener diode with a maximum power rating of 6W is connected across the output of the full-wave rectifier through a series resistor R_s to achieve the required voltage, calculate,

(i) The current that will flow through the Zener diode if a load resistor of $20k\Omega$ is connected across it [3marks]

(ii) The value of the series current-limiting resistor(R_s) [3marks]

(iii) The total load current(I_L) [3marks]

(iv) The total supply current(I_s) [3marks]

(c) A switching NPN silicon transistor has a forward current gain $\beta=100$ and maximum collector current $I_{c(max)}=25mA$. If the input voltage is 24V, calculate, the base resistor needed to switch the load "fully on". [4marks]

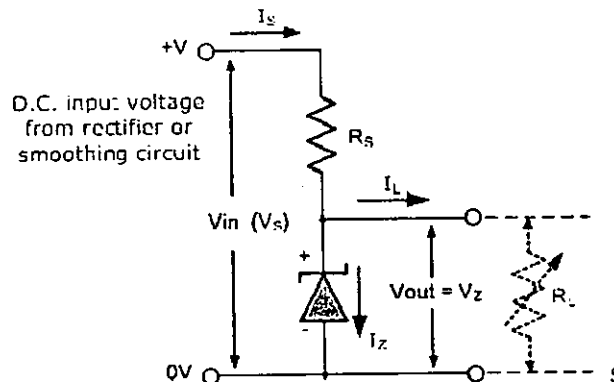


Figure 2

Q3 (a) Define the following parameters of power supply systems:

(i) Efficiency of rectification. [1 mark]

(ii) Ripple factor. [1 mark]

(iii) Peak inverse voltage(PIV) [1 mark]

(b) Draw a full-wave bridge rectifier with a capacitor input filter [2marks]

(c) With the aid of input and output waveforms briefly explain how the Q3(b) works. [3marks]

(d) A full-wave rectifier whose secondary voltage is 230V r.m.s has a load resistor of $200\text{k}\Omega$. Determine the following:

- (i) d.c output voltage [4marks]
- (ii) ripple voltage [4marks]
- (iii) PIV [4marks]

Q4 (a) State three general oscillator requirements [2marks]

(b) Explain briefly with the aid of diagram how oscillation is maintained in a simple LC tuned circuit. [3marks]

(c) Draw a circuit diagram of a crystal oscillator and explain how it works. [5marks]

(d) The electrical equivalent circuit of a crystal has a series inductance of 5H and a series capacitance of $25\mu\text{F}$. If the shunt capacitance is $100\mu\text{F}$, calculate the series and parallel resonant frequencies [4marks]

(e) Draw a circuit diagram of an Astable Multivibrator using Op Amp to generate the output signal [2marks]

(f) If the values of the external components are given as $R=24\text{k}\Omega$, $C=65\mu\text{F}$ and the regenerative feedback factor $\beta=0.01$, calculate the time period of the output waveform. [4marks]

Q5(a) The class of operation of an amplifier is very important. State the two bases upon which amplifiers are classified as class A, class B and class C. [2marks]

(b) Compare class A, class B and class C amplifiers in terms of:

(i) Overall Efficiency. [2marks]

(ii) Conduction Angle. [2marks]

(iii) Signal Distortion. [2marks]

(c) Give three types of Distortions associated with amplifiers [3marks]

(d) State in each case how the Distortion can be minimized [3marks]

(e) An amplifier has a gain of 60dB . If the input resistance of the amplifier is 75Ω and its output terminals feed a matched load of 140Ω , calculate the current that will flow in the load when a voltage of $100\mu\text{V}$ r.m.s is applied to the input terminals [6marks]