

University of Ghana  
(All rights reserved)

**BSc. Engineering**  
**First semester examinations: 2015/2016**  
**Department of Biomedical Engineering**  
**BMEN 303: Bioinstrumentation (3 credits)**

**INSTRUCTION:**


**Answer Three Questions in all (question 1 and any other two questions)**

**Time Allowed: 2 hrs 30 mins**

- 1a. Draw a well labelled diagram of an instrumentation amplifier and write down the expression for the output voltage  $V_o$ . (10 marks)
- b. Give three reasons why Instrumentation amplifiers (IA) are used in biomedical applications. (6 marks)
- c. Show that the overall gain of the circuit below is

$$V_o = \frac{R_2(V_b - V_a)}{R_1}$$

(9 marks)

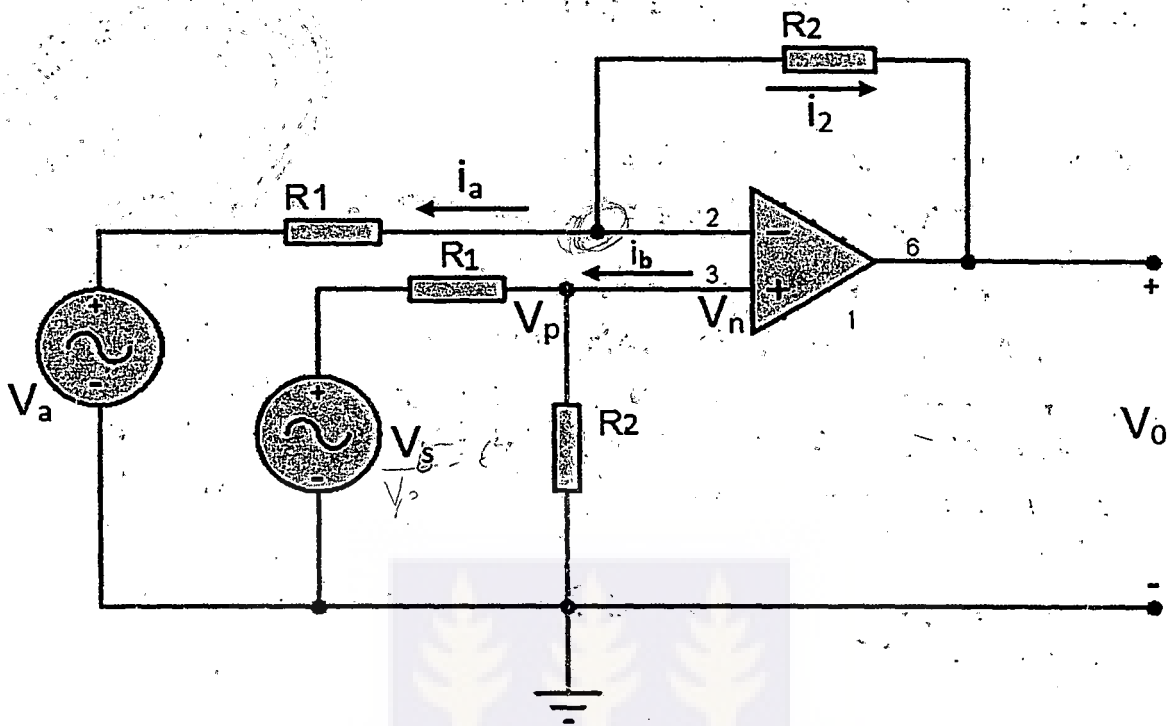

d. Sketch the circuit diagram of a non-inverting follower and calculate the voltage gain if  $R_1 = 2.2 \text{ k}\Omega$  and  $R_2 = 10 \text{ k}\Omega$ . (6 marks)

e. State two applications of the unity gain non-inverting follower. (4 marks)

f. Calculate the membrane potential of a cell at  $27^\circ \text{C}$  if the concentration of sodium ions in the cytoplasm and the extracellular fluid are  $13 \text{ mM}$  and  $110 \text{ mM}$ , respectively. Take Boltzmann's constant  $k$  to be  $1.38 \times 10^{-23} \text{ m}^2 \text{ kg s}^{-2} \text{ K}^{-1}$  and the charge  $q$  on an electron to be  $1.6 \times 10^{-19} \text{ C}$ . (6 marks)

2a. What is biopotential electrode? Give three reasons that made the  $\text{Ag}/\text{AgCl}$  electrode the most popular biopotential. (8 marks)

b. State the practical problems clinicians face when making biopotential measurements and state two ways how these problems are resolved. (8 marks)

c. Silver and aluminum electrodes are placed in an electrolyte solution. Calculate the current that will flow through the electrode if the equivalent resistance of the solution is  $2 \text{ k}\Omega$ . The Half-cell potentials for Silver and aluminum are  $0.799$  and  $-1.706 \text{ V}$  respectively. (6 marks)

d. Explain why amplifiers used in biomedical applications have very high input impedance. (3 marks)

e. What is motion artifact? Explain its effect on bio potential measurement. How is it reduced or eliminated? (5 marks)

3a. i. Explain the terms **impedance** and a **pole** in a filter design. (4 marks)

ii. By means of diagram only show how a simple passive RC low pass filter can be made. (6 marks)

iii. Under what conditions would you use a low pass filter? (4 marks)

b. Sketch and label the frequency response curve of a one pole low pass filter. (6 marks)

c. A low pass filter circuit of a resistor of  $47\text{ k}\Omega$  in series with a capacitor of  $47\text{ nF}$  is connected across a  $10\text{ V}$  sinusoidal supply. Sketch the circuit diagram and calculate the output voltage

( $V_{\text{out}}$ ) at frequency of  $100\text{ Hz}$  and a gain of 10. (10 marks)

4a. Draw a well labeled block diagram of a generalized instrumentation system and explain the function of each component. (10 marks)

b. State five problems in signal detection in living systems. (5 marks)

c. Sketch sample waveforms for the following biopotentials; ECG, EEG, EMG (6 marks)

i. State the most suitable electrode used in each case. (3 marks)

ii. The frequency range for each biopotential. (3 marks)

iii. Explain action potential of a cell. (3 marks)

