

**UNIVERSITY OF GHANA**

(All rights reserved)

BSC ENGINEERING/SECOND SEMESTER EXAMINATIONS: 2016/2017**SCHOOL OF ENGINEERING SCIENCES****FAEN 106: APPLIED ELECTRICITY (3 CREDITS)****INSTRUCTIONS:**

ANSWER ALL QUESTIONS IN SECTIONS A AND B AND THREE (3) QUESTIONS FROM SECTION C

SECTIONS A AND B ARE TO BE ANSWERED ON THE QUESTION SHEET

SECTION C SHOULD BE ANSWERED IN THE ANSWER BOOKLET PROVIDED

TIME ALLOWED: THREE (3) HOURS

SECTION A [20 MARKS]

Circle your choice of answer on the question paper.

1. In Ghana, power is transmitted at a linear frequency of 50 Hz which is equivalent to an angular frequency of
 - a) 314 s^{-1}
 - b) 50 s^{-1}
 - c) 314 rad s^{-1}
 - d) 50 rad s^{-1}
2. Electric current is simply the *rate of flow* of electric charge. Hence its unit could also be
 - a) C/s
 - b) J/s
 - c) J/C
 - d) A/s
3. To determine the *average value* of a symmetrical periodic waveform such as a sine wave, one can integrate the wave equation from:
 - a) 0 to 2π
 - b) $-\pi$ to π
 - c) $-\pi/2$ to $3\pi/2$
 - d) $-\pi$ to 0
4. The power dissipated in a $1.5\text{-k}\Omega$ pure resistor when a voltage $v = 200 \sin \omega t$ volts is applied across it is:
 - a) 300 kW
 - b) 26.67 W
 - c) 8.89 W
 - d) 13.33 W

5. In a RLC AC circuit, *heat dissipation* occurs through
 - a) Both the resistor and capacitor
 - b) Both the resistor and inductor
 - c) All three circuit elements
 - d) Only the resistor
6. In the derivation of the root mean square (RMS) value of a sine wave, we use the mean of the squares of the values (currents or voltages) because
 - a) Over one cycle the average value is zero
 - b) Over one cycle, the average value is too large
 - c) Over one cycle, the average value is too small
 - d) Over one cycle, the average value is constant.
7. A transformer is the main reason for the use of AC for electricity transmission. This is because
 - a) It has a very high efficiency and requires little or no maintenance over a long time
 - b) It is a very portable device
 - c) It is a purely resistive circuit
 - d) None of the above
8. The wiring in houses and buildings is arranged so all electric devices are in *parallel*. In this way if you disconnect one device,
 - a) The current to the others is not interrupted
 - b) The current to the others is interrupted
 - c) The whole circuit becomes open
 - d) A short circuit is created.
9. The effective resistance of an electric circuit that has a resistor $R \Omega$ in series with 10 resistors connected in parallel each also of resistance $R \Omega$ is:
 - a) $10R \Omega$
 - b) $11R \Omega$
 - c) $0.1R \Omega$
 - d) $1.1R \Omega$
10. Assuming your ECG bill for the month of September 2016 was GHC 135. What is the quantity of electricity consumed for the month if ECG charges 30 pesewas/unit and the service charge is also GHC 15?
 - a) 500 units
 - b) 150 units
 - c) 120 units
 - d) 400 units
11. A three-phase delta connected load has 30 A of current flowing through each phase winding. How much current is flowing through each of the lines supplying power to the load?
 - a) $30\sqrt{2}$ A
 - b) $30\sqrt{3}$ A
 - c) $30/\sqrt{3}$ A
 - d) 30 A
12. A three-phase delta connected load receives power from a supply of 560 V. How much voltage is dropped across each phase?
 - a) $560\sqrt{3}$ V
 - b) $560/\sqrt{3}$ V
 - c) 560 V
 - d) $560\sqrt{2}$ V

13. A three-phase wye-connected load has a phase current of 25 A. How much current is flowing through the lines supplying the load?
- a) $25/\sqrt{3}$ A
 - b) $25\sqrt{3}$ A
 - c) 25 A
 - d) $25\sqrt{2}$ A
14. A three-phase resistive load has a phase voltage of 240 V and a phase current of 18 A. What is the *total energy* consumed by this three-phase load in 10 h?
- a) 74.82 kWh
 - b) 129.6 kWh
 - c) 129600 kWh
 - d) 43.2 kWh
15. An alternating current completes 4 cycles in 5 ms. What is its frequency?
- a) 20 Hz
 - b) 125 Hz
 - c) 800 Hz
 - d) 0.02 Hz
16. In a simple *series* DC circuit, the following properties uniquely identify such a circuit.
- a) Same voltage drops across each series component but different currents
 - b) Each series component has the same value of current and voltage
 - c) Current is the same through each component but voltage drops are different
 - d) Voltage drops are the same as the source emf for each series component
17. For a simple DC circuit in which components are all connected in *parallel*:
- a) Current through each component is the same
 - b) Voltage across each component is the same as the source emf
 - c) Both the current and voltage values are the same for each component
 - d) None of the above
18. The impedance (Z) of a coil of resistance $4\ \Omega$ and reactance $3\ \Omega$ is:
- a) $7\ \Omega$
 - b) $25\ \Omega$
 - c) $5\ \Omega$
 - d) $1\ \Omega$
19. In electrical measurements, the unit of *conductance* is the:
- a) Ohm
 - b) Mho
 - c) Farad
 - d) Coulomb
20. Electric companies use a larger unit of electrical energy; the *kWh*, which is equivalent to:
- a) 36 MJ
 - b) 0.36 MJ
 - c) 3.6 MJ
 - d) 360 MJ

SECTION B [20 MARKS]

Answer all questions in this section on the question paper by filling in the blanks.

1. In a three-phase generator, the windings (phases) are degrees out of phase with each other.
2. In a single-phase power transmission, the power falls to zero times during each cycle.
3. In Ghana, the *peak value* of the *rms* voltage of 240 V that reaches our homes is
4. For a purely resistive three-phase circuit, the power of the circuit is $V_L * I_L$ using the parameters of line voltage and line current.
5. From Fig. SECBQ5, Kirchhoff's Current Law (KCL), indicates that $I_2 = \dots\dots\dots$

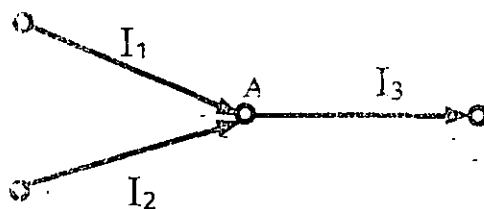


Fig. SECBQ5

6. According to KVL, in Fig. SECBQ6, $V_{R1} = \dots\dots\dots$

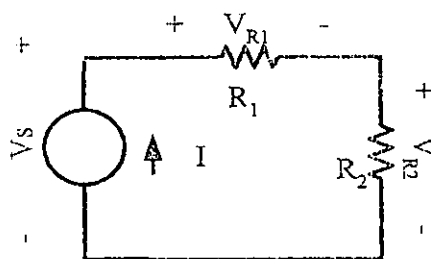


Fig. SECBQ6

7. In a circuit, an *ammeter* is connected in with the circuit components.
8. In a circuit, a *voltmeter* is connected in across the component whose p.d. it is to measure.
9. An Ohmmeter is used to measure the value of
10. The value of the resistance of a certain resistor from a certain manufacturer is rated $4.7 \text{ k}\Omega \pm 5\%$. The figure $\pm 5\%$ is called the
11. A transformer works by the Principle of Magnetic
12. The transformer experiences two main kinds of losses; these are and
13. The *effective value* of voltage or current in an AC circuit is commonly known as the value.
14. The units of the *resistivity* of a wire is
15. A piece of wire of diameter 4mm and length 10 mm and resistance 20Ω has resistivity
16. A three-phase circuit uses either wires or wires.
17. The *peak current* in a $1.8\text{-k}\Omega$ resistor connected to a 120-V rms ac source is
18. An open circuit has an resistance.

19. In a *capacitive* circuit, currentvoltage.

20. In an *inductive* circuit, current voltage.

SECTION C [60 MARKS]

Answer only three (3) questions from this section.

Each question carries 20 marks.

Q1.

- a) A single-phase network consists of three parallel branches, the currents in the respective branches being represented by:

$$i_1 = 20 \sin 314t \text{ amperes;}$$

$$i_2 = 30 \sin (314t - \pi/4) \text{ amperes;}$$

$$i_3 = 18 \sin (314t + \pi/2) \text{ amperes.}$$

The supply voltage for the network is also represented by $200 \sin 314t$ volts.

Calculate:

- i. The **total current** in a form similar to the branch currents; [3 marks]
 - ii. The **impedance, resistance, and reactance** of the network; [3 marks]
 - iii. The circuit **r.m.s.** current and **r.m.s.** voltage in **polar form**; [2 marks]
 - iv. The **apparent power** supplied by the sources in **polar form**; [2 marks]
 - v. The **apparent power** supplied by the sources in **rectangular (complex) form**; [2 marks]
 - vi. The **active power** absorbed and the **power factor** of the source. [2 marks]
- b) An alternating voltage v has a periodic time of 20 ms and a maximum value of 200 V. When time $t = 0$, $v = -75$ volts. Deduce a *sinusoidal expression* for v . If this alternating voltage feeds a $50 \angle 8^\circ \Omega$ impedance load, deduce a *sinusoidal expression* for the current, i , that is also generated. [6 marks]

Q2.

- a) Use a *delta-star conversion* to find the current I in the unbalanced bridge circuit in Fig. Q2a if the source voltage is 150 V . Hence determine the *rate of heat dissipation* from the $9\text{-}\Omega$ resistor and also from the *entire circuit* into the surrounding environment.

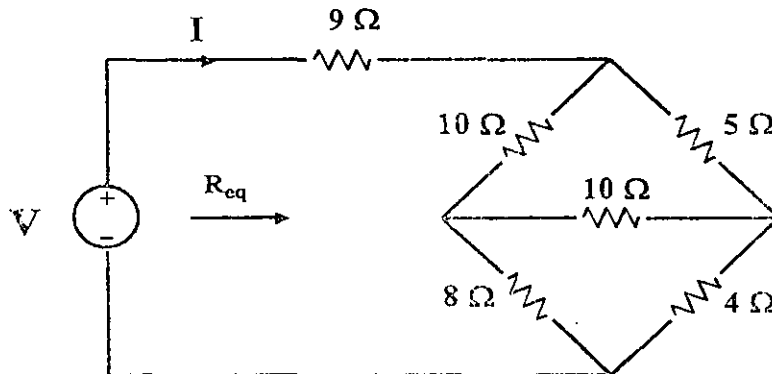


Fig. Q2a

[10 marks]

- b) Determine the equivalent resistance, R_T , of the circuit of Fig. Q2b.

[6 marks]

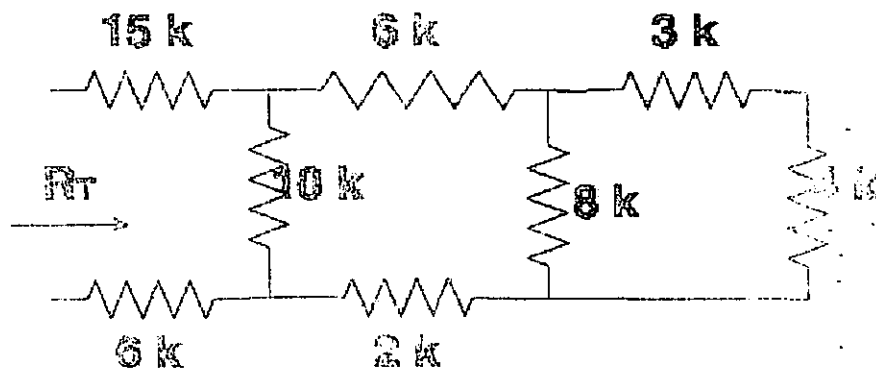


Fig. Q2b

Note the resistance values are in $\text{k}\Omega$.

- c) Two resistors when connected in series to a 110-V line use one fourth the power that is used when they are connected in parallel. If one resistor is $1.6\text{ k}\Omega$, what is the resistance of the other?

[4 marks]

Q3.

- a) A transformer is a magnetic circuit. Explain why this is so. [2 marks]
- b) A transformer has a turns ratio of 2:7. Explain this to a layman. [2 marks]
- c) State two (2) advantages and two (2) disadvantages of an auto-transformer. [4 marks]
- d) A transformer has 800 primary turns and 2000 secondary turns. If the primary voltage is 160 V, determine the secondary voltage assuming an ideal transformer. [2 marks]
- e) An ideal transformer connected to a 250 V mains, supplies a 25 V, 200 W lamp. Calculate the transformer turns ratio and the current taken from the supply. [4 marks]
- f) A model-train transformer plugs into 120 V ac and draws 0.65 A while supplying 15 A to the train. Calculate:
 - (i) the turns ratio of the transformer; [2 marks]
 - (ii) the voltage present across the tracks; and [2 marks]
 - (iii) the power transformed. [2 marks]

Q4.

- a) What is meant by three-phase (3- Φ) electric power? [2 marks]
- b) State *three advantages* of 3- Φ AC power over single-phase AC power. [3 marks]
- c) Three loads, each of resistance 50 Ω are connected in *star* to a 400 V, 3-phase supply. Determine:
 - i. The phase voltage; [1 mark]
 - ii. The phase current; and [1 mark]
 - iii. The line current. [1 mark]
- d) Three identical coils, each of resistance 10 Ω and inductance 42 mH are connected to a 415 V, 50 Hz, 3- Φ supply for *365 days*. Determine the *total energy* dissipated (kWh) when the coils are connected:
 - i. in star; and [3 marks]
 - ii. in delta. [3 marks]
- e) Purely resistive loads of 24 kW, 18 kW and 12 kW are connected between the neutral and the red, yellow and blue phases *respectively* of a 3- Φ , *four-wire* system. The line voltage is 415 V. Calculate:
 - i. The current in each line conductor (i.e., I_R , I_Y and I_B); and [3 marks]
 - ii. The current in the neutral conductor. [3 marks]

Q5.

- a) A motor takes a current of 10 A when supplied from a 250 V ac supply. Assuming a power factor of 0.75 lagging find the power consumed. Find also the cost of running the motor for 10 weeks continuously if 1 kWh of electricity costs 7.20 GHp. [5 marks]

- b) If four identical lamps are connected in parallel and the combined resistance is 100 Ω , find the resistance of one lamp. [2 marks]

- c) The instantaneous voltage in an AC circuit at any time t seconds is given by:
$$v = 100 \sin (50\pi t - 0.523) \text{ V.}$$

Find:

- i. the peak-to-peak voltage, the periodic time, the frequency and the phase angle; [2 marks]
 - ii. the voltage when $t = 0$; [1 mark]
 - iii. the voltage when $t = 8 \text{ ms}$; [1 mark]
 - iv. the time in the first cycle when the voltage is - 40 V; and [2 marks]
 - v. the first time when the voltage is a maximum. [2 marks]
- d) A load takes 50 kW at a power factor of 0.8 lagging. Calculate the *apparent power* and the *reactive power*. Determine the *capacitance* required to reduce the reactive power to *half of its original value* if the load is operating from a 250-V, 50-Hz supply. [5 marks]