



UNIVERSITY OF GHANA

(All rights reserved)

BSC. ENGINEERING

FIRST SEMESTER EXAMINATIONS: 2017/2018

DEPARTMENT OF BIOMEDICAL ENGINEERING

BMEN 303: BIOINSTRUMENTATION (3 CREDITS)

INSTRUCTIONS:

ANSWER FOUR (4) QUESTIONS

TIME ALLOWED: TWO AND HALF (2½) HOURS

1.

- a. Draw a well labeled diagram of an active high pass filter. (5 marks)
- b. An active filter has an op-amplifier as one of its components. State three uses of the amplifier. (3 marks)
- c. Sketch and label the frequency response curve of your diagram in 1a. (4 marks)
- d. Design a non-inverting active low pass filter circuit that has a gain of 10 at low frequencies, a high frequency cut-off or corner frequency of 159 Hz and an input impedance of 10 k Ω . (13 marks)

2.

- a. Mention five characteristics of ideal operational amplifier. (5 marks)
- b. A physical operational amplifier is not an ideal amplifier, draw a well labelled equivalent circuit diagram of an operational amplifier? (5 marks)
- c. Name three reasons why it is advantageous to include a negative feedback system in the design of a bio-amplifier. (3 marks)
- d. Design a non-inverting amplifier that has a gain of - 4, if the total resistance used is 100 k Ω . (12 marks)

3.

- a. Draw a block diagram of the instrumentation system used in EEG recording and briefly explain the function of each component. (8 marks)
- b. Brain waves are classified into four groups. Sketch and name samples of the brain waves with their dominant frequency range. (8 marks)
- c. Which one of the waves in 3b is the best known and most extensively studied? (2 marks)
- d. Name five applications of EEG. (5 marks)
- e. Name four sources of EEG artefacts. (2 marks)

4.

- a. What is meant by the mean arterial pressure (MAP) and what is its clinical significance? (4 marks)
- b. Three patients A, B and C have their blood pressure measured as 150/95, 110/40, and 83/50 respectively. Calculate each patient's MAP and comment on your results. (9 marks)
- c.
 - i. What is meant by slew rate? (2 marks)
 - ii. A 100 pF capacitor has maximum charging current of 150 μA . What is the slew rate? (5 marks)
 - iii. An operational amplifier has a slew rate of 2 V/ μs . If the peak output is 12 V, what is the power bandwidth? (5 marks)

5.

- a. In a tabular form or otherwise, mention **three biopotentials**, their sources, specifications, type of electrode used in measurement, source of error in measurement and selected applications? (15 marks)
- b. High input impedance and low output impedance are needed in the design of bio-amplifiers. Explain. (4 marks)
- c. What is the output voltage V_o for an input of 1.25 V in the circuit below? (6 marks)

