



UNIVERSITY OF GHANA
(All rights reserved)



BACHELOR OF SCIENCE IN ENGINEERING
SECOND SEMESTER EXAMINATIONS, 2011/2012
CPEN 202 DIGITAL SYSTEMS DESIGN (2 Credits)

TIME ALLOWED: TWO (2) HOURS


INSTRUCTION:

Answer ANY five (5) questions in your answer booklet.

Q1. Study the Truth Table below:

X_1	X_2	f
0	0	0
0	1	1
1	0	1
1	1	0

- L
- (i) Draw the circuit from this Truth Table. [7 Marks]
(ii) State one good use of this circuit. [3 Marks]
(iii) Write a VHDL code to implement your circuit. [10 Marks]
- Q2. (i) Explain how a Digital Combination Lock works. [5 Marks]
(ii) Using AND-Gates and Inverters, design a Digital Combination Lock whose input is 0110. [10 Marks]
(iii) Draw a state diagram for 0110. [5 Marks]
- Q3. (i) Draw and label the general block diagram of a synchronous sequential machine. [5 Marks]
(ii) Design the circuit for a sequential machine to detect 1010. [15 Marks]
- Q4. (i) From first principles, design a full Adder. [5 Marks]
(ii) Illustrate how a 4-bit Adder may be constructed. [5 Marks]
(iii) Write a VHDL code to implement the 4-bit Adder. [10 Marks]
- Q5. (i) Given the function $f(x_1, x_2, x_3) = \sum m(1, 4, 5, 6)$. Design a combinatorial circuit to implement this function. [10 Marks]
(ii) Write a VHDL code to implement your design. [10 Marks]

 

Q6.

Write short notes on the following:

- | | | |
|-------|-----------------------------|-----------|
| (i) | Testing. | [4 Marks] |
| (ii) | Stuck-at Fault. | [4 Marks] |
| (iii) | Fault Reductions. | [4 Marks] |
| (iv) | Fault Modeling and Testing. | [4 Marks] |
| (v) | Test Effectiveness. | [4 Marks] |

